

Question	Answer	Marks
1	C	1
2	B	1
3	B	1
4	$I = \frac{\Delta Q}{\Delta t} \Rightarrow \Delta Q = I\Delta t = 350 \times 10^{-3} \text{ A} \times 1 \text{ s} = 0.35 \text{ C}$ $Ne = \Delta Q \Rightarrow N = \frac{\Delta Q}{e} = \frac{0.35 \text{ C}}{1.6 \times 10^{-19}} = 2.1875 \times 10^{18} = 2.2 \times 10^{18} \text{ (2 s.f.)}$	1 1
5	<p>p.d. across 5.0Ω resistor = p.d. across terminals = 8.6 V</p> $R = \frac{V}{I} \Rightarrow I = \frac{V}{R} = \frac{8.6 \text{ V}}{5.0 \Omega} = 1.72 \text{ A}$ <p>p.d. across internal resistance r ('lost volts') $V_r = 9.0 \text{ V} - 8.6 \text{ V} = 0.4 \text{ V}$</p> $r = \frac{V_r}{I} = \frac{0.4 \text{ V}}{1.72 \text{ A}} = 0.2326 \Omega = 0.23 \Omega \text{ (2 s.f.)}$	1 1 1
6	$G = \frac{I}{V} = \frac{0.16 \text{ A}}{1.2 \text{ V}} = 0.1333 \text{ S}$ $G = \sigma \frac{A}{L} \Rightarrow \sigma = \frac{GL}{A}$ <p>Where $L = 0.85 \text{ m}$ and $A = \pi \times (0.05 \times 10^{-3} \text{ m})^2 = 7.854 \times 10^{-9} \text{ m}^2$</p> $\sigma = \frac{GL}{A} = \frac{0.1333 \text{ S} \times 0.85 \text{ m}}{7.854 \times 10^{-9} \text{ m}^2} = 1.443 \times 10^7 \text{ S m}^{-1} \text{ (2 s.f.)}$	1 1 1 1
7 a	$V_{\text{out}} = \frac{R_2}{R_1 + R_2} \times V_{\text{in}}$, where R_2 is the LDR, R_1 is the thermistor and $V_{\text{in}} = 4.5 \text{ V}$ $R_1 = 10 \text{ k}\Omega$ and $R_2 = 1000 \text{ k}\Omega$ under the conditions stated $V_{\text{out}} = \frac{1000 \text{ k}\Omega}{(100 \text{ k}\Omega + 1000 \text{ k}\Omega)} \times 4.5 \text{ V} = \frac{1000 \text{ k}\Omega}{1100 \text{ k}\Omega} \times 4.5 \text{ V} = 4.091 \text{ V} = 4.1 \text{ V}$ (2 s.f.)	1 1 1
7 b	R_2 will rise immediately while R_1 will be unchanged (it may rise a little, slowly) R_2 will now be a larger fraction of $(R_1 + R_2)$ So V_{out} will rise	1 1 1
8 a i	$P = IV = 10 \text{ A} \times 120 \text{ V} = 1200 \text{ W}$	1
8 a ii	$R = \frac{V}{I} = \frac{120 \text{ V}}{10 \text{ A}} = 12 \Omega$	1
8 b	$P = \frac{E}{\Delta t} \Rightarrow \Delta t = \frac{E}{P} = \frac{370 \times 10^3 \text{ J}}{1200 \text{ W}} = 308.3 \text{ s} = 310 \text{ s} \text{ (2 s.f.)}$	1
8 c	Assumption: resistance is the same Justification: temperature is kept the same by the water in the kettle $R = \frac{V}{I} \Rightarrow I = \frac{V}{R} = \frac{230 \text{ V}}{12 \Omega} = 19.17 \text{ A}$ $P = IV = 19.17 \text{ A} \times 230 \text{ V} = 4408 \text{ W}$ $\Delta t = \frac{E}{P} = \frac{370 \times 10^3 \text{ J}}{4408 \text{ W}} = 83.93 \text{ s} = 84 \text{ s} \text{ (2 s.f.)}$	1 1 1 1 1
8 d	Current drawn by the kettle $> 13 \text{ A}$ The kettle would blow a fuse/overheat and cause a fire.	1 1

9 a	Circuit should have: Battery of e.m.f. in range 1–20 V in series with thermistor and fixed resistor. Fixed resistor should be of value between 33 k Ω at 0 °C and 680 Ω . V_{out} measured across ends of fixed resistor.	1 1 1
9 b	Immerse thermistor and a thermometer in a water bath. Take regular readings of V_{out} over the range 0 °C (ice/water mix) to 100 °C (boiling). Plot calibration graph of V_{out} against temperature.	1 1 1
9 c	Calculate V_{out} , using the chosen value of fixed resistor and e.m.f., at 0 °C, 20 °C, 80 °C and 100 °C (all correct = 2 marks: at least one correct = 1 mark) (typical values, for $R_{\text{fixed}} = 10 \text{ k}\Omega$, are 1.0 V, 2.0 V, 4.0 V and 4.2 V respectively) Compare changes in V_{out} between 0 °C and 20 °C and between 80 °C and 100 °C. Recognise that sensitivity (change in p.d. per °C) is greater at lower temperatures.	2 1 1