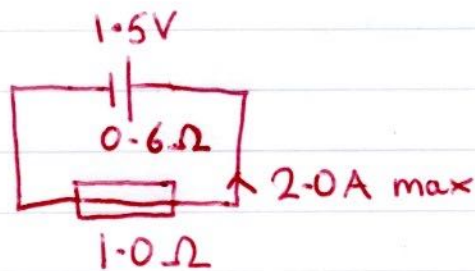


Resistors

① Fuse and resistors in series



$$1 \text{ cell } I = V/R = 1.5/(1.0+0.6) = 0.94 \text{ A OK}$$

$$2 \text{ cells } I = V/R = 3.0/(1.0+0.6+0.6) = 1.4 \text{ A OK}$$

$$3 \text{ cells } I = V/R = 4.5/(1.0+0.6+0.6+0.6) = 1.6 \text{ A OK}$$

$$4 \text{ cells } 1.5 \times 4 / (1 + (0.6 \times 4)) = 1.76 \text{ A OK}$$

OK fed up with this method so

$$I = \frac{V}{R} = \frac{1.5 \times n}{1 + 0.6n} < 2.0 \text{ A}$$

$$\frac{1.5n}{1 + 0.6n} < 2 \quad n = \text{number of cells.}$$


6 cells \Rightarrow 1.95 A
7 cells \Rightarrow 2.02 A

$$1.5n < 2 + 1.2n$$


$$0.3n < 2$$

$$n < 2/0.3 = 6.66 \text{ cells}$$

\therefore 6 cells max.

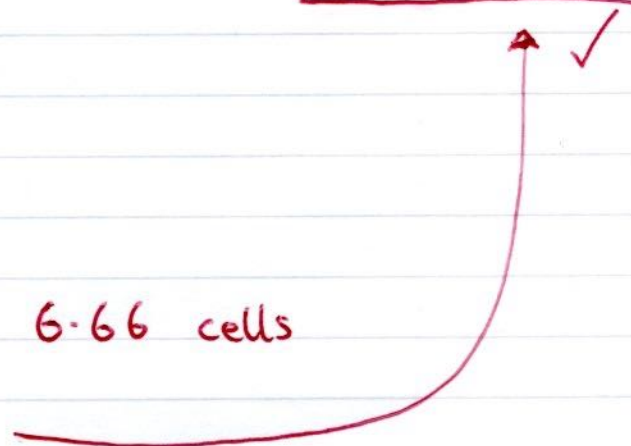

② Resistors in Parallel

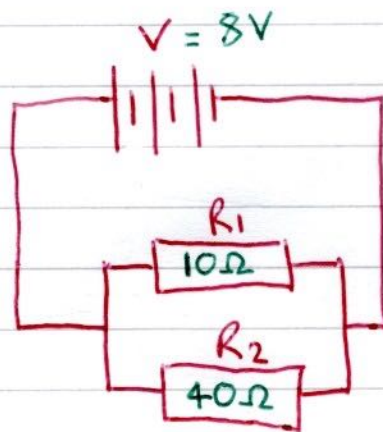

$$\textcircled{A} \quad \frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} = \frac{1}{10} + \frac{1}{40} = \frac{1}{8}$$

$$\therefore R_T = 8\Omega$$

$$I = V/R = 8V/8\Omega = \underline{1.0A}$$

$$\textcircled{B} \quad P = IR = V^2/R = 8^2/10 = \underline{6.4W}$$

③ Increases as resistance will be lower (or conductance will be higher)


④ For current to double the total resistance must halve so must now be 4Ω

$$\frac{1}{4} = \frac{1}{10} + \frac{1}{40} + \frac{1}{R_3}$$

$$\frac{1}{R_3} = \frac{1}{4} - \frac{1}{8} = \frac{1}{8}$$

$$\text{so } \underline{R_3 = 8\Omega}$$

③ Electron Current

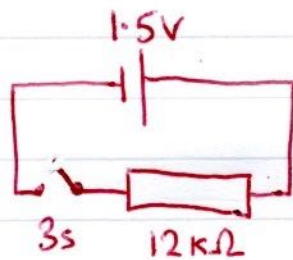


$$\text{Current} = V/R = 1.5/12 \times 10^3 = 1.25 \times 10^{-4} \text{ A}$$

$$\text{Charge} = It = 1.25 \times 10^{-4} \text{ A} \times 3 \text{ s} = 3.75 \times 10^{-4} \text{ C}$$

$$\text{No of electrons} = Q/e = \frac{3.75 \times 10^{-4} \text{ C}}{1.6 \times 10^{-19}} = \underline{2.3 \times 10^{15}}$$

④ Resistors in Parallel & Series

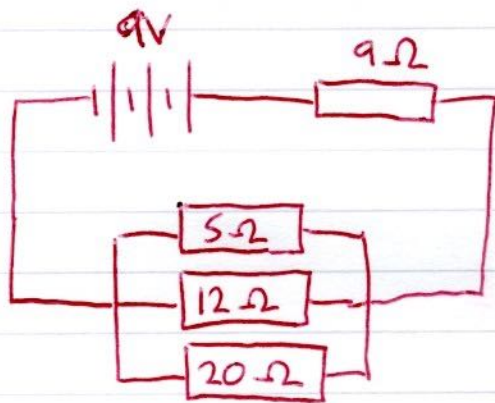

$$\text{A) } \frac{1}{R_T} = \frac{1}{5} + \frac{1}{12} + \frac{1}{20} = \frac{1}{3} \quad \therefore R_T = \underline{3 \Omega}$$

$$\text{B) } I = V/R = \frac{9\text{V}}{9\Omega + 3\Omega} = 0.75 \text{ A} \\ = \underline{0.8 \text{ A}} \quad \text{1st}$$

$$\text{C) Voltage across } 5\Omega \text{ resistor} = \frac{3}{9+3} \times 9\text{V} = 2.25\text{V}$$

$$\text{Current} = V/R = 2.25\text{V}/5\Omega = 0.45\text{A} = \underline{0.5\text{A}}$$

⑤ Power of a light bulb.


Bulb 2.0V \rightarrow 0.3A

4.0V \rightarrow 0.5A

6.0V \rightarrow 0.6A

(from graph)

①

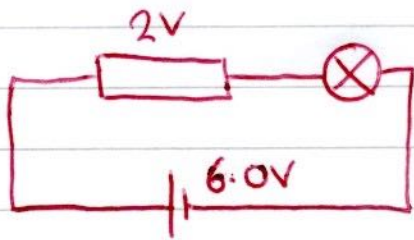

① If 2V across resistor 4V must be across lamp.
so the current must be 0.5A


$$P = IV = 0.5A \times 4V = 2.0W$$

② If current is 0.30A then voltage across bulb must be 2.0V so voltage across resistor must be 4.0V.

$$R = V/I = 4.0V / 0.3A = 13.3 \Omega$$

13 Ω 2 sf.

⑥ Two cells & two resistors

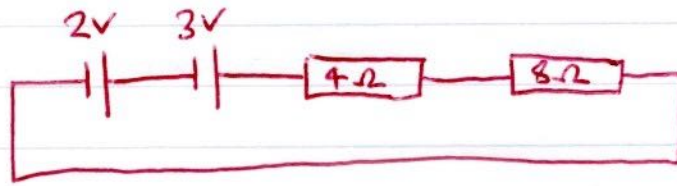


① $R_T = 4\Omega + 8\Omega = 12\Omega$

wrong way cell $\Rightarrow 1V \quad \therefore I = V/R = \frac{1V}{12\Omega} = 0.08A$

correct way cell $\Rightarrow 5V \quad \therefore I = V/R = \frac{5V}{12\Omega} = 0.42A$

\downarrow Ratio = 5.0 ← or

⑦ Range of related resistors

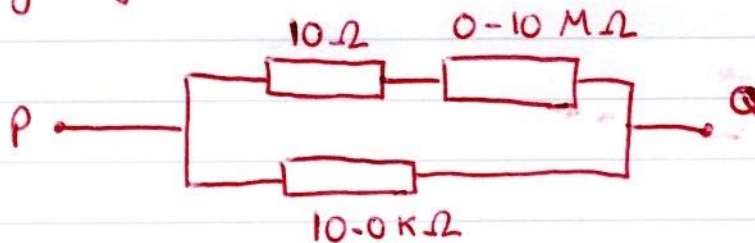

max $\frac{10000010\Omega}{10000\Omega} = 9990.01\Omega$


A circuit diagram for maximum resistance. It shows a 10Ω resistor and a $10M\Omega$ resistor in series, connected in parallel with a $10k\Omega$ resistor. The total resistance is calculated as $\frac{10000010\Omega}{10000\Omega} = 9990.01\Omega$.

min $\frac{10\Omega}{10k\Omega} = 9.99001\Omega$

A circuit diagram for minimum resistance. It shows a 10Ω resistor and a $10k\Omega$ resistor connected in parallel. The total resistance is calculated as $\frac{10\Omega}{10k\Omega} = 9.99001\Omega$.

Difference = 9980Ω


⑧ Cells in Reverse

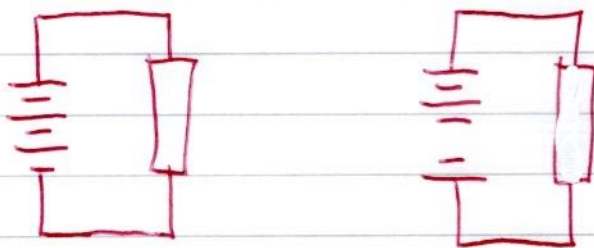

voltage ratio = 3:1 \therefore power ratio = 9:1

as $P = IV = I^2R = V^2/R$ and R is constant so $P \propto V^2 = 3^2 = 9$


⑨ Series resistors

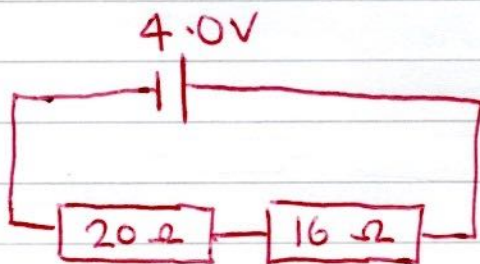

① $R_T = 20\Omega + 16\Omega = 36\Omega$

$I = V/R = 4.0V / 36\Omega = 0.11A$

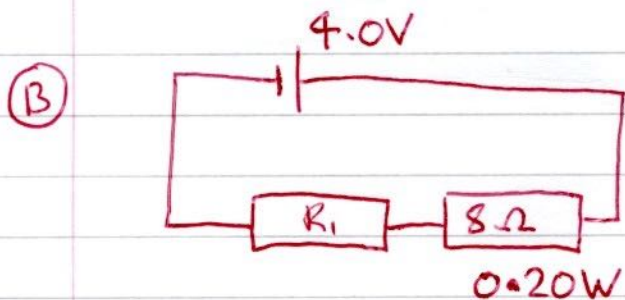$P = I^2R = 0.11^2 \times 16 = 0.198W$
 $= 0.20W$ 2 sf




$P = I^2R \therefore I = \sqrt{P/R} = \sqrt{\frac{0.20}{8}}$
 $= 0.158A$

TOTAL $R = V/I = 4 / 0.158 = 25.3\Omega$

17.3Ω

$\therefore R_1 = 25.3 - 8 = 17.3\Omega$

⑩ Current in parallel Resistors

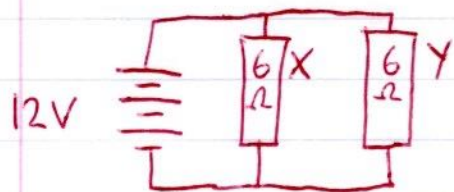

$$X, Y = 6\ \Omega$$

$$\text{Combined resistance} = \frac{1}{R_T} = \frac{1}{6} + \frac{1}{6} = \frac{1}{3}$$

$$\therefore R_T = 3\ \Omega$$

$$I_{\text{TOTAL}} = 12\text{V}/R = 12/3 = 4.0\text{A}$$

$$\therefore \text{current through each} = 4.0\text{A}/2 = \underline{2.0\text{A}}$$

$$\text{or just } I = V/R = 12/6 = \underline{2.0\text{A}}$$

↑
ie much more simply!