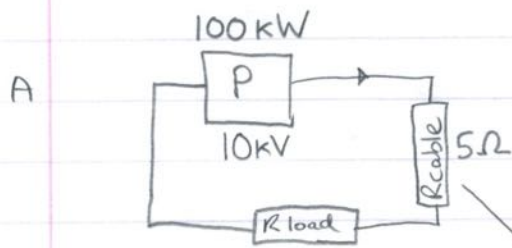


Resistances: Issac Physics

SA answers.

① Power loss in cables



$$P = IV$$


$$I = P/V = \frac{100 \times 10^3 \text{ W}}{10 \times 10^3 \text{ V}} = 10 \text{ A}$$

$$P = IV = I^2 R = 10 \text{ A}^2 \times 5 \Omega = 500 \text{ W}$$

B

$$E_{\text{eff}} = \frac{100 \times 10^3 - 500 \text{ W}}{100 \times 10^3 \text{ W}} \times 100 = 99.5\%$$

② Finding internal resistance

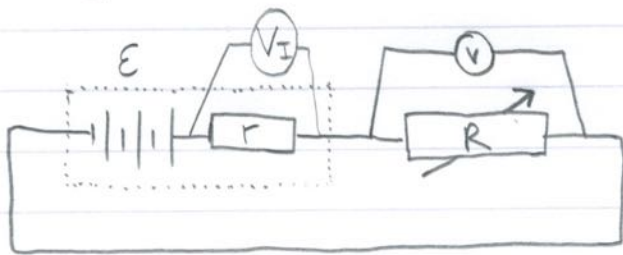

$$R = 2.0 \Omega, V = 6.0 \text{ V} \quad I = V/R = \frac{6.0}{2.0} = 3.0 \text{ A}$$

$$R = 4.0 \Omega, V = 8.0 \text{ V} \quad I = V/R = \frac{8.0}{4.0} = 2.0 \text{ A}$$

$$\mathcal{E} = V_I + V \quad \& \quad V_I = Ir$$

so $\mathcal{E} = V + Ir$


$$\therefore 8 + 2.0 \times r = 6 + 3.0 \times r$$

$$2 + 2r = 3r$$

$$2 = r$$

$$r = 2.0 \Omega$$


③ Current and resistance

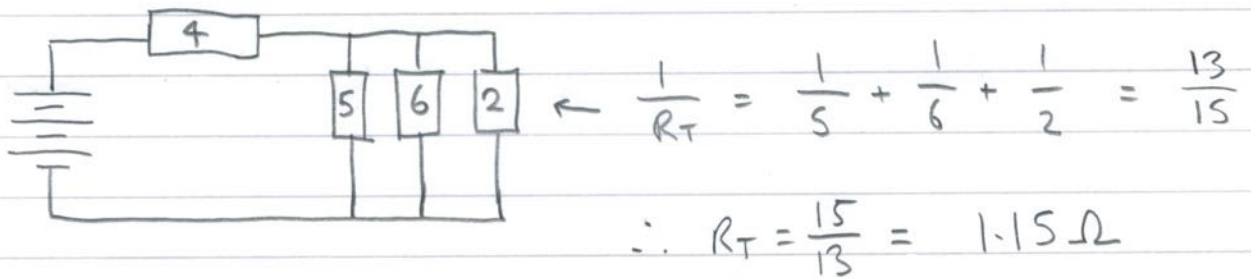

so total R of circuit = $4 + 1.15 \Omega = 5.15 \Omega$

$$I = V/R = 10/5.15 = 1.9 A$$

④ Vital Voltmeters

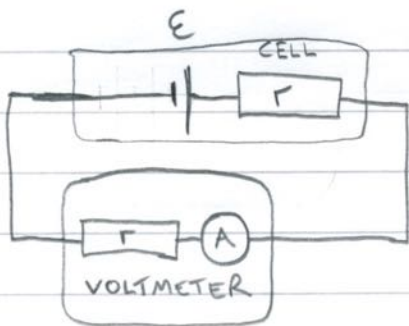


A Voltmeter P has resistance $r \Omega$ so ϵ is shared equally across two resistances $\rightarrow \epsilon/2$

Voltmeter Q has resistance $10r \Omega$ so most of ϵ is across it \rightarrow nearly ϵ

\therefore 2nd option
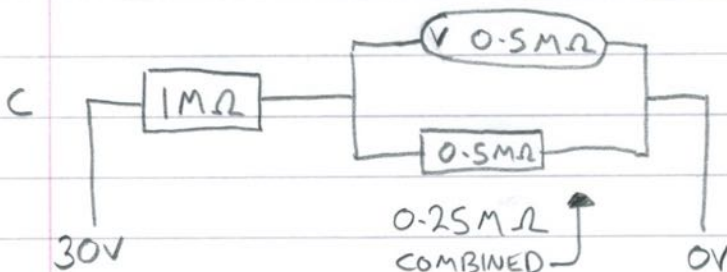
$$B \quad V = V_{in} \frac{R_2}{R_1 + R_2} = 30V \times \frac{0.5}{1 + 0.5} = 10V$$



$$V = V_{in} \frac{R_2}{R_1 + R_2} = 30 \times \frac{0.25}{1 + 0.25} = 6.0V$$

⑤ Melting a Snowman

Ⓐ $P = IV = 0.23A \times 6.0V = 1.4W$

Ⓑ $V = \frac{4}{3}\pi r^3 = \frac{4}{3}\pi \times 0.5^3 + \frac{4}{3}\pi \times 1.0^3$
 $= 4.712 \text{ m}^3$

$m = v \times d = 4.712 \text{ m}^3 \times 930 \text{ kg m}^{-3}$
 $= 4400 \text{ Kg}$

Ⓒ At 30% efficiency \rightarrow 70% Heat


so heating power = $0.70 \times 1.4W = 0.98W$

Energy to melt = $4400 \text{ kg} \times 1000 \times 335 \text{ J/g}$
 $= 1.47 \times 10^9 \text{ J}$


$E = Pt \quad \therefore t = E/p = \frac{1.47 \times 10^9}{0.98} = 1.5 \times 10^9 \text{ s}$

In years $\frac{1.5 \times 10^9}{60 \times 60 \times 24 \times 365.25}$
 $= 48 \text{ years}$


⑥ Heating an Electric Fire

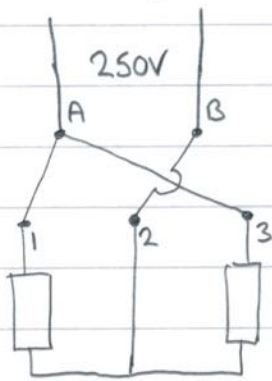

3.0 kW

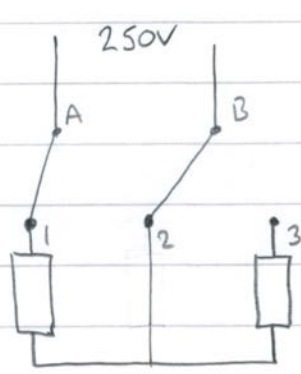

1.5 kW

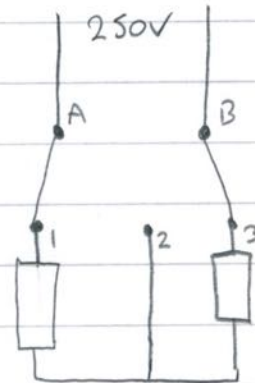

0.75 kW

$$P = IV$$

$$I = \frac{V}{R}$$

$$\therefore P = \frac{V^2}{R}$$

$$R = \frac{V^2}{P}$$

$$R = \frac{250^2}{3 \times 10^3} = 21 \Omega, \quad R = \frac{250^2}{1.5 \times 10^3} = 42 \Omega, \quad R = \frac{250^2}{0.75 \times 10^3} = 83 \Omega$$

must be
in parallel

eg.
A=1 & 3
+
B=2

must be
single

eg.
A=1 B=2

must be in
series

eg.
A=1 B=3

- Ⓐ First Answer
- Ⓑ Last Answer
- Ⓒ Third Answer
- Ⓓ 42 Ω

⑦ Conveying Current

Each second...

A  $A = 5\text{m} \times 0.1\text{m} = 0.5\text{m}^2$

$$e \text{ density} = 1 \times 10^4 \text{ per mm}^2 = 1 \times 10^{10} \text{ per m}^2$$

$$\text{so No of electrons} = 0.5\text{m}^2 \times 1 \times 10^{10} \text{m}^{-2} = 5 \times 10^9$$

$$e = 1.6 \times 10^{-19} \text{ C} \quad \therefore Q = 1.6 \times 10^{-19} \times 5 \times 10^9 = 8 \times 10^{-10} \text{ C}$$


$$\therefore I = 8.0 \times 10^{-10} \text{ A}$$

B 3000 protons cancel out 3000 electrons per mm^2

$$\begin{aligned} \text{so effective number of electrons} &= 0.5 \times 0.7 \times 10^{10} \\ &= 3.5 \times 10^9 \text{ electrons} \end{aligned}$$

$$I = 3.5 \times 10^9 \times 1.6 \times 10^{-19} = 5.6 \times 10^{-10} \text{ A}$$


⑧ Power in Resistors

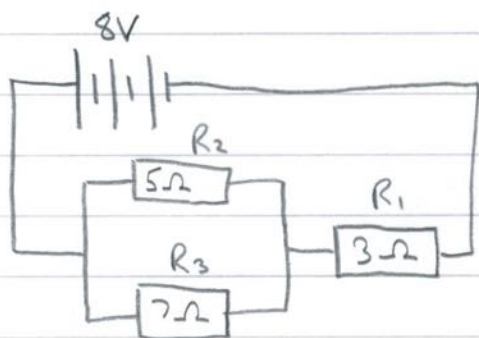

$$\text{Overall resistance} = 3 + \frac{1}{\frac{1}{5} + \frac{1}{7}} = 5.92 \Omega$$

① $P = IR$ & $I = V/R$ $\therefore P = V^2/R = 8^2/5.92 = 11\text{W}$

② $\text{Current} = V/R = 8/5.92 = 1.35\text{A}$

Combined resistance of  = $\frac{1}{1/5 + 1/7} = 2.9 \Omega$

so voltage approx shared equally across them and the 3Ω

$\therefore 5\Omega \quad P \approx 4^2/5 \approx 3.2\text{W}$


$7\Omega \quad P \approx 4^2/7 \approx 2.3\text{W}$

$3\Omega \quad P \approx 4^2/3 \approx 5.3\text{W}$

so R_1 dissipates most power

③ $P = I^2 R = 1.35^2 \times 3.0 = 5.5\text{W}$


9) Resistors with tolerance

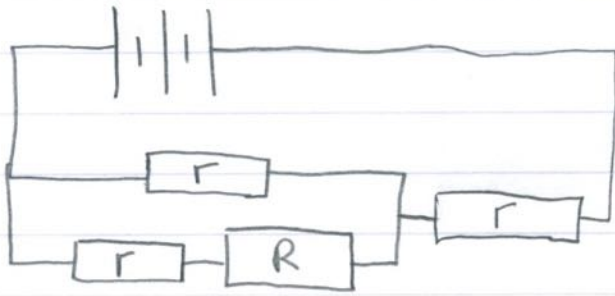

$$r = 5.0\Omega \pm 20\% = 5.0\Omega \pm 1\Omega$$

$$\text{min} = 4.0\Omega \quad \text{max} = 6.0\Omega$$

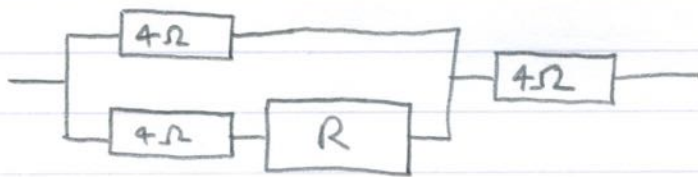Need to ensure $I \leq 1.0\text{A}$ worst case scenario is when all r s are 4.0Ω



If $I \leq 1.0\text{A}$ then $R_{\text{TOTAL}} \geq 7.0\Omega$ as $I = \frac{V}{R}$

and $\frac{7\text{V}}{7\Omega} = 1\text{A}$.

\therefore must = or exceed 3Ω


$$\therefore \frac{1}{3\Omega} = \frac{1}{4\Omega} + \frac{1}{4\Omega + R}$$

$$\therefore \frac{1}{4+R} = \frac{1}{3} - \frac{1}{4} = \frac{1}{12}$$

$$\therefore 4+R = 12 \quad \therefore R = 8.0\Omega \quad \text{but } R \text{ is } \pm 20\%$$

$$\therefore \frac{8.0}{0.8} = \underline{\underline{10\Omega}} \quad (\pm 20\% \text{ has lowest value of } 8\Omega)$$

10) Power limited resistors

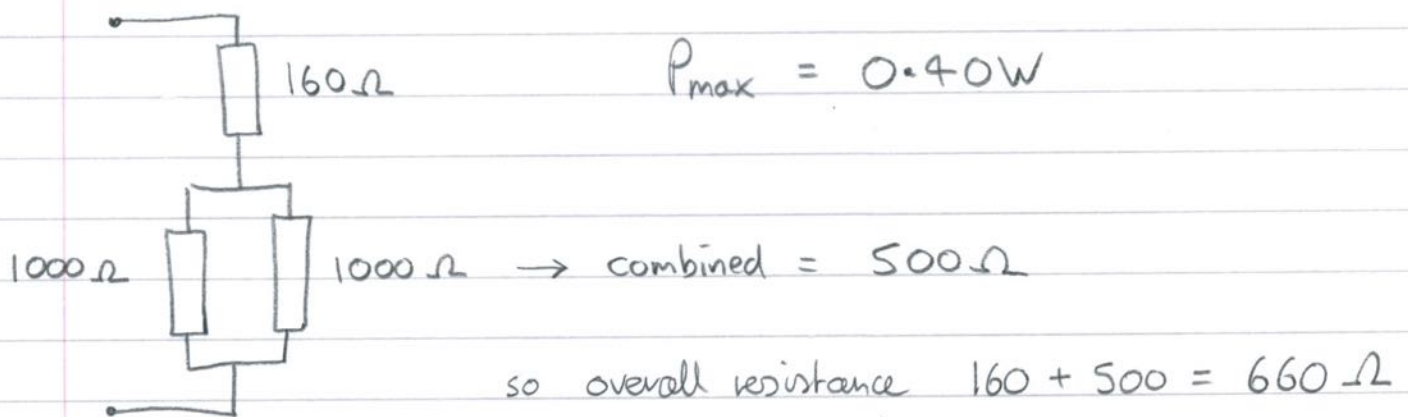

$$\textcircled{A} \quad V_{160\Omega} = V_T \times \frac{160}{660} \quad V_{1000\Omega} = V_T \times \frac{500}{660}$$

$$P = IV = \frac{V_T 160 I}{660} = \frac{V_T 500 I}{660 \times 2}$$

↑ half current

$$= \frac{160}{660} V_T I = \frac{250}{660} V_T I$$

↑
higher power so 1000Ω
will fail first

$$\textcircled{B} \quad P = I^2 R \quad \therefore$$

$$I_{1000} = \sqrt{P/R} = \sqrt{0.4/1000} = 0.02A \text{ each}$$

$I_{1000 \text{ total}} = 0.04A$

$$V = IR = 0.04A \times 660\Omega = 26V$$